

20

$$R = 5 \Omega$$

$$I = 2 \text{ A}$$

$$P = ?$$

$$P = I^2 R$$

$$= (2)^2 \times 5$$

$$P = 4 \times 5$$

$$P = 20 \text{ W}$$


14/06/2023

### Tutorial 6

Question 1 is in the SAD tutorial section.

- 9) Three resistors  $6 \Omega$ ,  $12 \Omega$ , and  $4 \Omega$  are connected in series to an electric supply of  $12 \text{ V}$ .

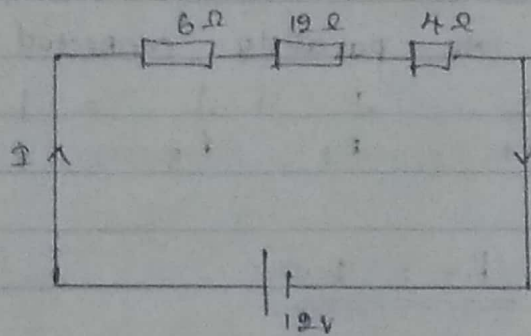- (i) Calculate the total resistance of these three resistors.




$$R_T = 6 + 12 + 4 = 22 \Omega //$$

- (ii) What is the current from the electric supply?

$$V = IR$$

$$I = \frac{V}{R} = \frac{12}{22} = \frac{6}{11} \text{ A} = \underline{\underline{0.55 \text{ A}}}$$

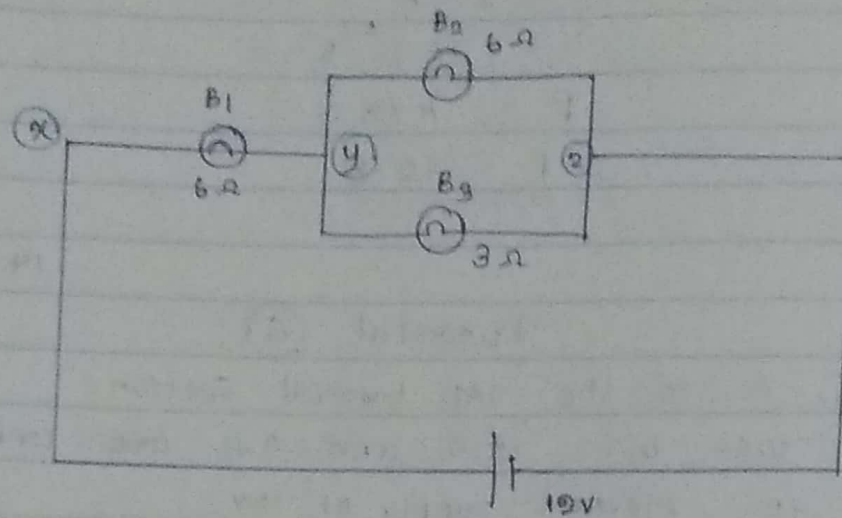- ⑧ Three bulbs,  $B_1$ ,  $B_2$ ,  $B_3$  are connected to 12V supply as shown in the following diagram.



- ① Calculate the total resistance of the two bulbs  $B_2$  and  $B_3$  (between y and z)  
 $B_2$  and  $B_3$  are parallelly connected to each other  
 $\therefore \frac{1}{R_T} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{6} + \frac{1}{3} = \frac{2}{6} = \frac{1}{3}$

$$\underline{R_T = 3\Omega}$$

- ② What is the total resistance between the two points x and z.



$$R_{T'} = 6 + 2\Omega$$

$$\underline{R_{T'} = 8\Omega}$$

- ③ What is the current gained from the electricity supply?

$$V = IR$$

$$I = \frac{V}{R} = \frac{12}{8} = \frac{6}{4} = \frac{3}{2} = 1.5$$

$$I = 1.5A //$$

iv) Calculate the potential difference between x and y.

$$P = VI$$

$$P = I^2 R$$

$$= (1.5)^2 \times 6$$

$$= \left(\frac{3}{2}\right)^2 \times 6 = \frac{9}{4} \times 6 = \frac{27}{2}$$

$$P = 13.5 \text{ W}$$


v) Calculate the potential difference between y and z.

$$P = VI$$


$$= I^2 R$$

$$= \frac{9}{4} \times 2$$

$$P = 4.5 \text{ W}$$

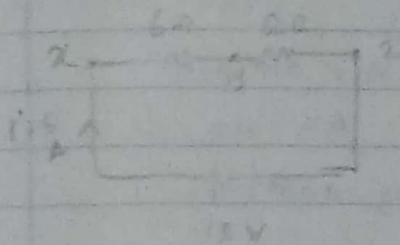

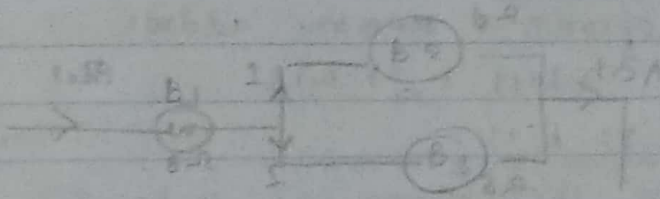vi) Calculate the current flow through  $B_2$  &  $B_3$ .



$$\frac{1.5 \times 1}{3} = \frac{1}{2} = 0.5 \text{ A}$$


$$\frac{1.5 \times 2}{3} = \frac{1}{2} \times 2 = 1 \text{ A}$$

$$I_{B2} = 0.5 \text{ A}$$

$$I_{B3} = 1 \text{ A}$$

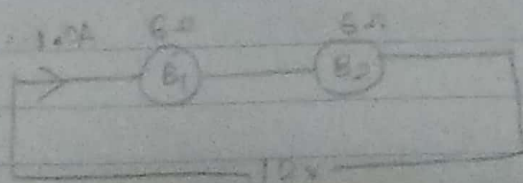viii) If  $B_3$  is removed, then what would be the current gain from the electric supply.

$$I = \frac{V}{R} = \frac{12}{12} = 1 \text{ A}$$





If bit =  $n \rightarrow$

no. of functions =  $n^2$   
it will allow

consider 4 bit opcode

$$n = 4$$

$$4^2 = 16$$

4 bit opcode will allow 16 different functions.

Tutorial 7

### Quick Review Question 1

- Consider a computer that is used for simple numerical problems. It uses 9 bits for an opcode and 25 bits for a memory address.

a) What is the size of its instructions?  
34 bits

$$\begin{aligned}\text{Instruction size} &= \text{opcode} + \text{memory address} \\ &= 9 \text{ bits} + 25 \text{ bits} \\ &= \underline{34 \text{ bits}}\end{aligned}$$

b) How many different instructions can it have?  
 $2^9 = 512$  bits

c) What is the maximum memory size that it can address?  
 $2^{25} / 2^{20} = 32 \text{ M}$   
(Note: Assume that  $2^{20}$  is about 1M)